

$$= 12 \Omega$$

WS-14 for class 6th

Basic

① Given $i = 0.2 \text{ A}$

$$R = 10 \Omega$$

$$E = 2.1 \text{ V}$$

$$i = \frac{E}{r + R}$$

$$\Rightarrow 0.2 = \frac{2.1}{r + 10}$$

$$\Rightarrow r + 10 = \frac{2.1}{0.2} = 10.5$$

$$\Rightarrow r = 0.5 \Omega$$

② $E_1 = 3 \text{ V}; E_2 = 2 \text{ V}$

$$E_{\text{eff}} = E_1 + E_2 = 3 + 2 = 5 \text{ V}$$

③ Given $E_1 = 3 \text{ V}; E_2 = 2 \text{ V}$

$$i = 10 \text{ A} \quad i = \frac{E_1 + E_2}{R}$$

$$\Rightarrow 10 = \frac{3 + 2}{R}$$

$$\Rightarrow R = \frac{5}{10} = 0.5 \Omega$$

④ $n = 6; m = 2$

$$E.m.f = (n - 2m)E$$

$$= (6 - 2 \times 2)E$$

$$= (6 - 4)E$$

$$= 2E$$

⑤ $n = 4; E.m.f = 2 \text{ V}$

$$r = 1 \Omega; R = 6 \Omega$$

$$\frac{1}{r_{\text{eff}}} = \frac{1}{r} + \frac{1}{r} + \frac{1}{r} + \frac{1}{r}$$

$$r_{\text{eff}} = \frac{1}{4} = 0.25 \Omega$$

$$i = \frac{E.m.f}{T.R_{\text{eff}}} = \frac{2}{6 + 0.25}$$

⑥

$$i = 0.1 \text{ A} \quad i = \frac{E}{r + R}$$

$$\Rightarrow 0.1 = \frac{1.5}{r + 10}$$

$$\Rightarrow r + 10 = 15$$

$$\Rightarrow r = 5 \Omega$$

⑦ $n = 3$; NO. of combinations = 2^n

$$= 2^3 = 8$$

⑧ $n = 4$; NO. of combinations = 2^n

$$= 2^4 = 16$$

also

⑨ $E_1 = 2 \text{ V}$

$$r_1 = 1 \Omega$$

$$R = 5 \Omega$$

$$E_2 = 4 \text{ V}$$

$$r_2 = 0.5 \Omega$$

$$E.m.f \text{ of the combination} = \frac{E_1}{r_1} + \frac{E_2}{r_2}$$

$$= \frac{2}{1} + \frac{4}{0.5} = \frac{2 + 8}{1 + 0.5}$$

$$E = \frac{10}{3} = 3.33 \text{ V}$$

⑩ Along with

Total resistance in circuit

$$= \frac{1}{r_1} + \frac{1}{r_2} + R$$

$$= 1 + \frac{1}{0.5} + 5 = 1 + 2 + 5$$

$$= 8 \Omega$$

$$i = \frac{E}{T.R} = \frac{3.33}{8} = 0.416 \text{ A}$$



(15) $E = 10V$; $r = 3\Omega$

(16) $E_1 = 10V$; $E_2 = 30V$

(17) $E = 50V$; $r = 10\Omega$

Total e.m.f

$E = E_1 + E_2$

$= 10 + 30$

$= 40V$

$R = 10\Omega$ $i = 4.5A$

$i = \frac{E}{R+r} \Rightarrow 4.5 = \frac{50}{10+r}$

$\Rightarrow 10+r = \frac{50}{4.5} = \frac{500}{45} = 11.1$

$\Rightarrow r = 1.1\Omega$

$R = 17\Omega$; $i = 0.5A$

Total Resistance = $R+r$

$= 17 + 3$

$= 20\Omega$

(ii) $V = E - ir$

$= 10 - 0.5 \times 3$

$= 10 - 1.5$

$\Rightarrow 8.5V$

Task

(1) $n = 4$; $E = 1V$
 $m = 1$ $r = 0.5\Omega$; $R = 1\Omega$

$i = \frac{E_{total}}{R} = \frac{(n-2m)E}{nr + R}$

$i = \frac{(4-2 \times 1) \times 1}{4 \times 0.5 + 1} = \frac{2}{2+1}$

$i = \frac{2}{3}A$

(2) $E = 2V$; $n = 12$
 $m = 3$

$E.m.f = (n-2m)E$

$= (12-2 \times 3) \times 2$

$= (12-6) \times 2$

$= 12V$

(4) Here two cells are identical, if they are connected in parallel. e.m.f = constant
Their effective e.m.f = $20V$

(5) Given $R_1 = 16\Omega$; $V_1 = 12V$

$V_1 = E - i_1 r$

$R_2 = 10\Omega$; $V_2 = 11V$

$V_2 = E - i_2 r \rightarrow (1)$

$V_2 = E - i_2 r \Rightarrow 11 = E - i_2 r \rightarrow (2)$

By doing (1) - (2) $\Rightarrow 12 - 11 = E - i_1 r - E + i_2 r$

$\Rightarrow 1 = i_2 r - i_1 r \Rightarrow i = \frac{V_2}{R_2} r - \frac{V_1}{R_1} r$

$\Rightarrow 1 = \left[\frac{11}{10} - \frac{12}{16} \right] r \Rightarrow r = \frac{20}{7}\Omega$

(6) Given $E_1 = 2V$; $E_2 = 4V$; $E_3 = 6V$

Effective e.m.f $E = E_1 + E_2 + E_3$

$= 2 + 4 + 6 = 12V$

(7) No. of wires are $n = 5$

No. of combination = $2^{n-1} = 2^{5-1} = 2^4 = 16$

(3) $E_1 = 1.25V$; $E_2 = 0.75V$

$r_1 = r_2 = 1\Omega$

Since both cells are having same internal resistance so high e.m.f in e.m.f of combination $e.m.f = 1.25V$

(8) $n = 5$; $r = 6\Omega$

Effective resistance = nr

In series combination $= 5 \times 6 = 30\Omega$

(9) Given $r_1 = 0.3 \Omega$, $E_1 = 2V$

$r_2 = 0.6 \Omega$, $E_2 = 3V$

$$E.m.f = \frac{E_1 + E_2}{\frac{1}{r_1} + \frac{1}{r_2}}$$

$$= \frac{2 + 3}{\frac{1}{0.3} + \frac{1}{0.6}}$$

$$= \frac{5}{\frac{1}{0.3} + \frac{1}{0.6}}$$

By solving it

$$E.m.f = \frac{2.1}{0.9} = \frac{2.1}{0.9} = \frac{7}{3}$$

$$= 2.33V$$

(10) Given $E = 5V$, $n = 10$

$$m = 3$$

$$\text{Effective } e.m.f = (n - 2m)E$$

$$= (10 - 2 \times 3) \times 5$$

$$= (10 - 6) \times 5$$

$$= 4 \times 5$$

$$= 20V$$

(15) (i) Given $E_A = E_V = 2.4V$

$$R = 1 \Omega$$

Total internal resistance

$$\text{of combination} = \frac{1}{r_1} + \frac{1}{r_2} + R$$

$$= \frac{1}{0.9} + \frac{1}{0.9} + 1 = 3.8$$

(ii) $i = \frac{E.m.f}{3.8} = \frac{4}{3.8} = 1.054$

(16) $n = 5$, $R = 1$

Effective resistance of parallel combination

$$R_p = \frac{R}{n} = \frac{1}{5} = 0.2 \Omega$$

(17) Here 6 cells are identical and are connected in parallel. Effective $e.m.f = \text{constant} = 6V$.

